

The Basic Elements and Phasors

14.1 INTRODUCTION

The response of the basic R , L , and C elements to a sinusoidal voltage and current will be examined in this chapter, with special note of how frequency will affect the “opposing” characteristic of each element. Phasor notation will then be introduced to establish a method of analysis that permits a direct correspondence with a number of the methods, theorems, and concepts introduced in the dc chapters.

14.2 THE DERIVATIVE

In order to understand the response of the basic R , L , and C elements to a sinusoidal signal, you need to examine the concept of the derivative in some detail. It will not be necessary that you become proficient in the mathematical technique, but simply that you understand the impact of a relationship defined by a derivative.

Recall from Section 10.11 that the derivative dx/dt is defined as the rate of change of x with respect to time. If x fails to change at a particular instant, $dx = 0$, and the derivative is zero. For the sinusoidal waveform, dx/dt is zero only at the positive and negative peaks ($\omega t = \pi/2$ and $3\pi/2$ in Fig. 14.1), since x fails to change at these instants of time. The derivative dx/dt is actually the slope of the graph at any instant of time.

A close examination of the sinusoidal waveform will also indicate that the greatest change in x will occur at the instants $\omega t = 0, \pi$, and 2π . The derivative is therefore a maximum at these points. At 0 and 2π , x increases at its greatest rate, and the derivative is given a positive sign since x increases with time. At π , dx/dt decreases at the same rate as it increases at 0 and 2π , but the derivative is given a negative sign since x decreases with time. Since the rate of change at 0, π , and 2π is the same, the magnitude of the derivative at these points is the same also. For various values of ωt between these maxima and minima, the derivative will exist and will have values from the minimum to the maximum inclusive. A plot of the derivative in Fig. 14.2 shows that

the derivative of a sine wave is a cosine wave.

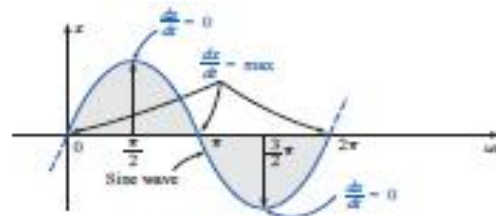


FIG. 14.1
Defining those points in a sinusoidal waveform that have maximum and minimum derivatives.

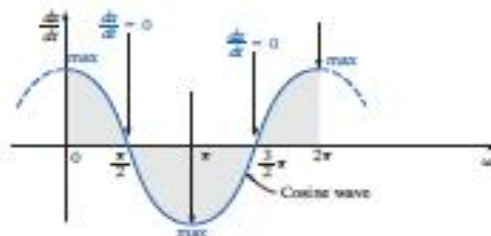


FIG. 14.2
Derivative of the sine wave of Fig. 14.1.

The peak value of the cosine wave is directly related to the frequency of the original waveform. The higher the frequency, the steeper the slope at the horizontal axis and the greater the value of dx/dt , as shown in Fig. 14.3 for two different frequencies.

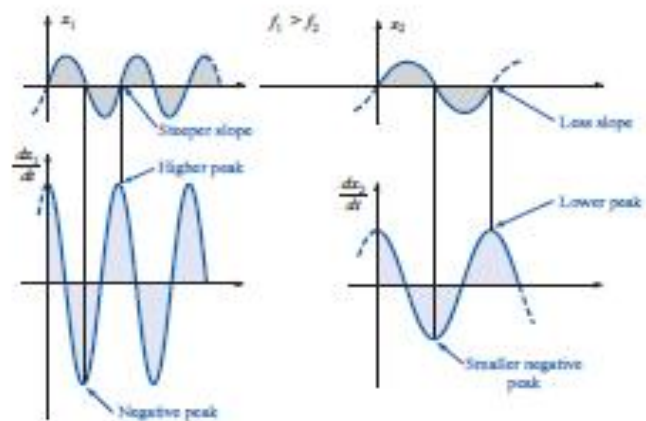


FIG. 14.3
Effect of frequency on the peak value of the derivative.

Note in Fig. 14.3 that even though both waveforms (x_1 and x_2) have the same peak value, the sinusoidal function with the higher frequency produces the larger peak value for the derivative. In addition, note that *the derivative of a sine wave has the same period and frequency as the original sinusoidal waveform.*

For the sinusoidal voltage

$$e(t) = E_m \sin(\omega t \pm \theta)$$

the derivative can be found directly by differentiation (calculus) to produce the following:

$$\frac{d}{dt} e(t) = \omega E_m \cos(\omega t \pm \theta) = 2\pi f E_m \cos(\omega t \pm \theta) \quad (14.1)$$

The mechanics of the differentiation process will not be discussed or investigated here; nor will they be required to continue with the text. Note, however, that the peak value of the derivative, $2\pi f E_m$, is a function of the frequency of $e(t)$, and the derivative of a sine wave is a cosine wave.

14.3 RESPONSE OF BASIC R, L, AND C ELEMENTS TO A SINUSOIDAL VOLTAGE OR CURRENT

Now that we are familiar with the characteristics of the derivative of a sinusoidal function, we can investigate the response of the basic elements R , L , and C to a sinusoidal voltage or current.

Resistor

For power-line frequencies and frequencies up to a few hundred kilohertz, resistance is, for all practical purposes, unaffected by the frequency of the applied sinusoidal voltage or current. For this frequency region, the resistor R of Fig. 14.4 can be treated as a constant, and Ohm's law can be applied as follows. For $v = V_m \sin \omega t$,

$$i = \frac{v}{R} = \frac{V_m \sin \omega t}{R} = \frac{V_m}{R} \sin \omega t = I_m \sin \omega t$$

where

$$I_m = \frac{V_m}{R} \quad (14.2)$$

In addition, for a given i ,

$$v = iR = (I_m \sin \omega t)R = I_m R \sin \omega t = V_m \sin \omega t$$

where

$$V_m = I_m R \quad (14.3)$$

A plot of v and i in Fig. 14.5 reveals that

for a purely resistive element, the voltage across and the current through the element are in phase, with their peak values related by Ohm's law.

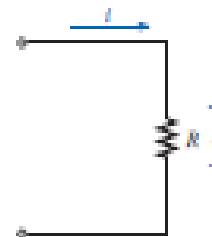


FIG. 14.4 Determining the sinusoidal response for a resistive element.

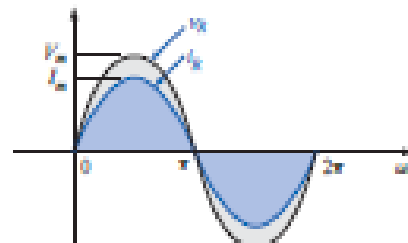


FIG. 14.5 The voltage and current of a resistive element are in phase.

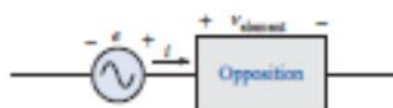


FIG. 14.6

Defining the opposition of an element to the flow of charge through the element.

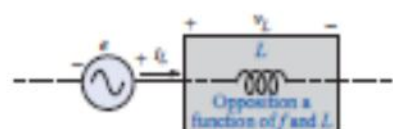


FIG. 14.7

Defining the parameters that determine the opposition of an inductive element to the flow of charge.

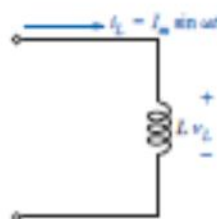


FIG. 14.8

Investigating the sinusoidal response of an inductive element.

Inductor

For the series configuration of Fig. 14.6, the voltage v_{element} of the boxed-in element opposes the source e and thereby reduces the magnitude of the current i . The magnitude of the voltage across the element is determined by the opposition of the element to the flow of charge, or current i . For a resistive element, we have found that the opposition is its resistance and that v_{element} and i are determined by $v_{\text{element}} = iR$.

We found in Chapter 12 that the voltage across an inductor is directly related to the rate of change of current through the coil. Consequently, the higher the frequency, the greater will be the rate of change of current through the coil, and the greater the magnitude of the voltage. In addition, we found in the same chapter that the inductance of a coil will determine the rate of change of the flux linking a coil for a particular change in current through the coil. The higher the inductance, the greater the rate of change of the flux linkages, and the greater the resulting voltage across the coil.

The inductive voltage, therefore, is directly related to the frequency (or, more specifically, the angular velocity of the sinusoidal ac current through the coil) and the inductance of the coil. For increasing values of f and L in Fig. 14.7, the magnitude of v_L will increase as described above.

Utilizing the similarities between Figs. 14.6 and 14.7, we find that increasing levels of v_L are directly related to increasing levels of opposition in Fig. 14.6. Since v_L will increase with both $\omega (= 2\pi f)$ and L , the opposition of an inductive element is as defined in Fig. 14.7.

We will now verify some of the preceding conclusions using a more mathematical approach and then define a few important quantities to be employed in the sections and chapters to follow.

For the inductor of Fig. 14.8, we recall from Chapter 12 that

$$v_L = L \frac{di_L}{dt}$$

and, applying differentiation,

$$\frac{di_L}{dt} = \frac{d}{dt}(I_m \sin \omega t) = \omega I_m \cos \omega t$$

Therefore, $v_L = L \frac{di_L}{dt} = L(\omega I_m \cos \omega t) = \omega L I_m \cos \omega t$

or

$$v_L = V_m \sin(\omega t + 90^\circ)$$

where

$$V_m = \omega L I_m$$

Note that the peak value of v_L is directly related to $\omega (= 2\pi f)$ and L , as predicted in the discussion above.

A plot of v_L and i_L in Fig. 14.9 reveals that

for an inductor, v_L leads i_L by 90° , or i_L lags v_L by 90° .

If a phase angle is included in the sinusoidal expression for i_L , such as

$$i_L = I_m \sin(\omega t \pm \theta)$$

then

$$v_L = \omega L I_m \sin(\omega t \pm \theta + 90^\circ)$$

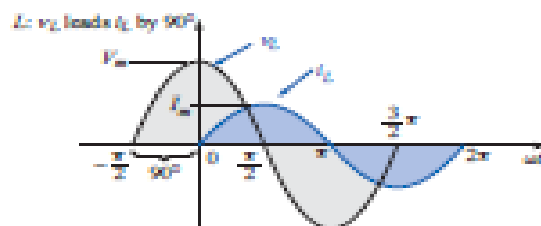


FIG. 14.9

For a pure inductor, the voltage across the coil leads the current through the coil by 90° .

The opposition established by an inductor in a sinusoidal ac network can now be found by applying Eq. (4.1):

$$\text{Effect} = \frac{\text{cause}}{\text{opposition}}$$

which, for our purposes, can be written

$$\text{Opposition} = \frac{\text{cause}}{\text{effect}}$$

Substituting values, we have

$$\text{Opposition} = \frac{V_m}{I_m} = \frac{\omega l I_m}{I_m} = \omega l$$

revealing that the opposition established by an inductor in an ac sinusoidal network is directly related to the product of the angular velocity ($\omega = 2\pi f$) and the inductance, verifying our earlier conclusions.

The quantity ωl , called the reactance (from the word *reaction*) of an inductor, is symbolically represented by X_L and is measured in ohms; that is,

$$X_L = \omega l \quad (\text{ohms}, \Omega) \quad (14.4)$$

In an Ohm's law format, its magnitude can be determined from

$$X_L = \frac{V_m}{I_m} \quad (\text{ohms}, \Omega) \quad (14.5)$$

Inductive reactance is the opposition to the flow of current, which results in the continual interchange of energy between the source and the magnetic field of the inductor. In other words, inductive reactance, unlike resistance (which dissipates energy in the form of heat), does not dissipate electrical energy (ignoring the effects of the internal resistance of the inductor).

Capacitor

Let us now return to the series configuration of Fig. 14.6 and insert the capacitor as the element of interest. For the capacitor, however, we will determine i for a particular voltage across the element. When this approach reaches its conclusion, the relationship between the voltage

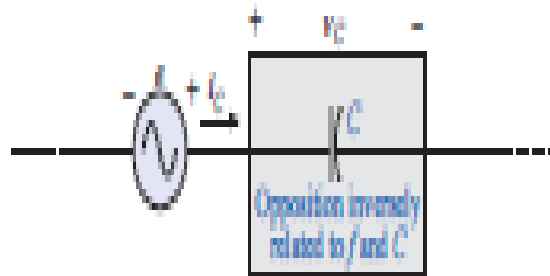


FIG. 14.10

Defining the parameters that determine the opposition of a capacitive element to the flow of the charge.

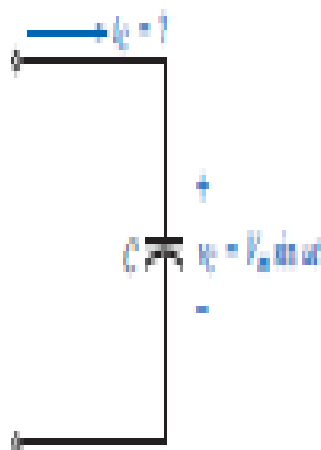


FIG. 14.11

Investigating the sinusoidal response of a capacitive element.

We will now verify, as we did for the inductor, some of the above conclusions using a more mathematical approach.

For the capacitor of Fig. 14.11, we recall from Chapter 10 that

$$i_C = C \frac{dv_C}{dt}$$

and, applying differentiation,

$$\frac{dv_C}{dt} = \frac{d}{dt}(V_m \sin \omega t) = \omega V_m \cos \omega t$$

Therefore,

$$i_C = C \frac{dv_C}{dt} = C(\omega V_m \cos \omega t) = \omega C V_m \cos \omega t$$

or
$$i_C = I_m \sin(\omega t + 90^\circ)$$

where
$$I_m = \omega C V_m$$

Note that the peak value of i_C is directly related to ω ($= 2\pi f$) and C , as predicted in the discussion above.

A plot of v_C and i_C in Fig. 14.12 reveals that

for a capacitor, i_C leads v_C by 90° , or v_C lags i_C by 90° .

If a phase angle is included in the sinusoidal expression for v_C , such as

$$v_C = V_m \sin(\omega t \pm \theta)$$

then
$$i_C = \omega C V_m \sin(\omega t \pm \theta + 90^\circ)$$

Applying

$$\text{Opposition} = \frac{\text{cause}}{\text{effect}}$$

and substituting values, we obtain

$$\text{Opposition} = \frac{V_m}{I_m} = \frac{V_m}{\omega C V_m} = \frac{1}{\omega C}$$

which agrees with the results obtained above.

The quantity $1/\omega C$, called the reactance of a capacitor, is symbolically represented by X_C and is measured in ohms; that is,

$$X_C = \frac{1}{\omega C} \quad (\text{ohms}, \Omega) \quad (14.6)$$

In an Ohm's law format, its magnitude can be determined from

$$X_C = \frac{V_m}{I_m} \quad (\text{ohms}, \Omega) \quad (14.7)$$

Capacitive reactance is the opposition to the flow of charge, which results in the continual interchange of energy between the source and the electric field of the capacitor. Like the inductor, the capacitor does *not* dissipate energy in any form (ignoring the effects of the leakage resistance).

In the circuits just considered, the current was given in the inductive circuit, and the voltage in the capacitive circuit. This was done to avoid the use of integration in finding the unknown quantities. In the inductive circuit,

$$v_L = L \frac{di_L}{dt}$$

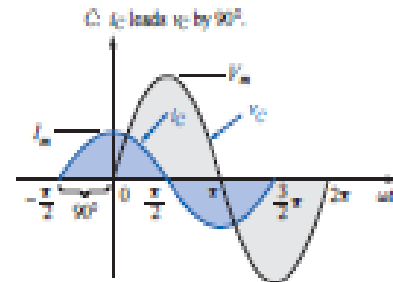


FIG. 14.12

The current of a purely capacitive element leads the voltage across the element by 90° .

but
$$i_L = \frac{1}{L} \int v_L dt \quad (14.8)$$

In the capacitive circuit,

$$i_C = C \frac{dv_C}{dt}$$

but
$$v_C = \frac{1}{C} \int i_C dt \quad (14.9)$$

Shortly, we shall consider a method of analyzing ac circuits that will permit us to solve for an unknown quantity with sinusoidal input without having to use direct integration or differentiation.

It is possible to determine whether a network with one or more elements is predominantly capacitive or inductive by noting the phase relationship between the input voltage and current.

If the source current leads the applied voltage, the network is predominantly capacitive, and if the applied voltage leads the source current, it is predominantly inductive.

Since we now have an equation for the reactance of an inductor or capacitor, we do not need to use derivatives or integration in the examples to be considered. Simply applying Ohm's law, $I_m = E_m/X_L$ (or X_C), and keeping in mind the phase relationship between the voltage and current for each element, will be sufficient to complete the examples.

EXAMPLE 14.1 The voltage across a resistor is indicated. Find the sinusoidal expression for the current if the resistor is 10Ω . Sketch the curves for v and i .

- $v = 100 \sin 377t$
- $v = 25 \sin(377t + 60^\circ)$

Solutions:

a. Eq. (14.2): $I_m = \frac{V_m}{R} = \frac{100 \text{ V}}{10 \Omega} = 10 \text{ A}$

(v and i are in phase), resulting in

$$i = 10 \sin 377t$$

The curves are sketched in Fig. 14.13.

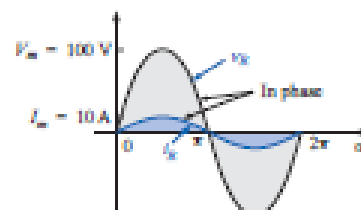


FIG. 14.13
Example 14.1(a).

b. Eq. (14.2): $I_m = \frac{V_m}{R} = \frac{25 \text{ V}}{10 \Omega} = 2.5 \text{ A}$

(v and i are in phase), resulting in

$$i = 2.5 \sin(377t + 60^\circ)$$

The curves are sketched in Fig. 14.14.

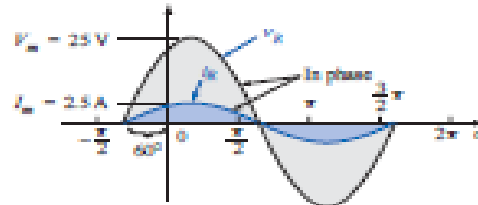


FIG. 14.14
Example 14.1(b).

EXAMPLE 14.2 The current through a $5\text{-}\Omega$ resistor is given. Find the sinusoidal expression for the voltage across the resistor for $i = 40 \sin(377t + 30^\circ)$.

Solution: Eq. (14.3): $V_m = I_m R = (40 \text{ A})(5 \Omega) = 200 \text{ V}$

(v and i are in phase), resulting in

$$v = 200 \sin(377t + 30^\circ)$$

EXAMPLE 14.3 The current through a 0.1-H coil is provided. Find the sinusoidal expression for the voltage across the coil. Sketch the v and i curves.

a. $i = 10 \sin 377t$

b. $i = 7 \sin(377t - 70^\circ)$

Solutions:

a. Eq. (14.4): $X_L = \omega L = (377 \text{ rad/s})(0.1 \text{ H}) = 37.7 \Omega$

Eq. (14.5): $V_m = I_m X_L = (10 \text{ A})(37.7 \Omega) = 377 \text{ V}$

and we know that for a coil v leads i by 90° . Therefore,

$$v = 377 \sin(377t + 90^\circ)$$

The curves are sketched in Fig. 14.15.

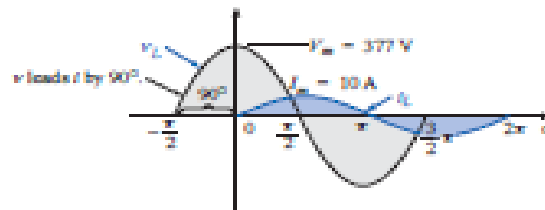


FIG. 14.15
Example 14.3(a).