#### DC load line

The cut-off point for this line is where  $V_{CE}=V_{CC}$ . It is also written as  $V_{CE}$  (cut-off) saturation point is given by  $I_C=V_{CC}/R_L$ . It is represented by straight line AQB in Fig.1.

## AC load line

The cut-off point is given by  $V_{CE(cut-off)} = V_{CEQ} + I_{CQ}R_{ac}$ , where  $R_{ac}$  is the ac

load resistance. Saturation point is given by  $I_{C(sat)} = I_{CQ} + V_{CEQ}/R_{ac}$ .

It is represented by straight line CQD in Fig.1. The slope of the ac load line is given by  $y=-1/R_{ac}$ .

It is seen from Fig. 1 that maximum possible positive signal swing is =  $I_{CQ}R_{ac}$ . Similarly, maximum possible negative signal swing is  $V_{CEQ}$ .

**Example:** Draw the dc and ac load lines for the CE circuit shown in fig. below, (a) what is the maximum peak to peak signal that can be obtained?

Solution:

#### **DC load line**

V<sub>CE(cut-off)</sub>=V<sub>CC</sub>=20V. (point A)

 $I_{C(Sat)} = V_{CC}/(R_L + R_E) = 20/5 = 4mA$  (point B).

Hence, AB represents dc load line for the given circuit.

Approximate bias conditions can be quickly found by assuming that  $I_B$  is too small to affect the base bias as in fig. below  $V_2 = 20 \times 4/(4 + 16) = 4$  V. If we neglect  $V_{BE}$ ,  $V_2 = V_E$ ;

$$I_E = \frac{V_E}{R_E} = \frac{V_2}{R_E} = \frac{4}{2}$$
$$= 2 \text{ mA}$$

Also,  $I_C \approx I_E = 2$  mA. Hence,  $I_{CQ} = 2$  mA.

#### AC Load Line

Cut-off point,  $V_{CE(cut-off)} = V_{CEQ} + I_{CQ}R_{ac}$ 

Now, for the given circuit, ac load resistance is  $R_{ac} = R_C = 3K$ .

Cut-off point =  $10 + 2 \times 3 = 16$  V. Saturation point,

$$I_{c(sat)} = I_{QQ} + \frac{V_{CEQ}}{R_{ac}} = 2 + \frac{10}{3} = 5.13 \,\mathrm{mA}$$

Hence, line joining 16-V point and 5.13 mA. Point gives ac load line as shown in Fig. (b). As expected, this line passes through the Q-point.

Now,  $I_{CQ}$ .  $R_{ac} = 2 \times 3 = 6$  V and  $V_{CEQ} = 10$  V. Taking the smaller quantity, maximum peak output signal = 6 V. Hence, peak-to-peak value =  $2 \times 6 = 12$  V.



#### What are h-parameter?

These are four constants which describe the behavior of a two-port linear network. A linear network is one in which resistance, inductances and capacitances remain fixed when voltage across them is changed.

Consider an unknown linear network contained in a black box as shown in Fig. 1. As a matter of convention, currents flowing into the box are taken positive whereas those flowing out of it are considered negative.



Similarly, voltages are positive from the upper to the lower terminals and negative the other way around. The electrical behavior of such a circuit can be described with the help of four hybrid parameters or constants designated as  $h_{ll}$ ,  $h_{l2}$ ,  $h_{2l}$ ,  $h_{2l}$ .

In this type of double-number subscripts, it is implied that the first variable is always divided by the other. The subscript 1 refers to quantities on the input side and 2 to the quantities on the output side. The letter 'h' has come from the word hybrid which mixture of distinctly different items. These constants are hybrid because they have different units. Out of the four h-parameters, two are found by short-circuiting the output terminals 2-2 and the other two by open-circuiting the input terminals 1-1 of the circuit.

(a) Finding  $h_{11}$  and  $h_{21}$  from Short-Circuit Test

As shown in Fig. , the output terminals have been shorted so that  $v_2 = 0$ , because no voltage can exist on a short.

The linear circuit within the box is driven by an input voltage  $v_1$ . It produces an input current  $i_1$  whose magnitude depends on the type of circuit within the box.





These two constants are known as forward parameters. The constant  $h_{11}$  represents input impedance with output shorted and has the unit of ohm. The constant  $h_{21}$  represents current gain of the circuit with output shorted and has no unit since it is the ratio of two similar quantities.

The voltages and currents of such a two-port network are related by the following sets of equations or V/I relations

$$V_1 = h_{11}i_1 + h_{12}V_2$$
  
$$i_2 = h_{21}i_1 + h_{22}V_2$$

Here, the hare constants for a given circuit but change if the circuit is changed. Knowledge of parameters enables us to find the voltages and currents with the help of the above two equations.

(b) Finding  $h_{12}$  and  $h_{22}$  from Open-circuit Test

As shown in Fig.3, the input terminals are open so that  $i_1 = 0$  but there does appear a voltage  $v_1$  across them. The output terminals are driven by an ac voltage  $v_2$  which sets up current  $i_2$ .



As seen,  $h_{12}$  represents voltage gain (not forward gain which is  $v_2 / v_1$ ). Hence, it has no units. The constant  $h_{22}$  represents admittance (which is reverse of resistance) and has the unit of mho or Siemens, s.

It is actually the admittance looking into the output terminals with input terminals open. Generally, these two constants are also referred to as reverse parameters.

Summary of h-parameters  

$$h_{11} = \text{ input impedance}$$
  
 $h_{21} = \text{ forward current gain}$   
 $h_{12} = \text{ reverse voltage gain}$   
 $h = \text{ output admittance}$   
with output shorted

# The h-parameter Notation for Transistors

While using h-parameters for transistor circuits, their numerical subscripts are replaced by the first letters for defining them.

$$\begin{array}{c} h_{11} = h_i = \text{input impedance} \\ h_{21} = h_f = \text{forward current gain} \end{array} \quad \text{output shorted} \\ \hline \\ h_{12} = h_r = \text{reverse voltage gain} \\ \hline \\ h_{22} = h_0 = \text{output admittance} \end{array} \quad \text{input open}$$

A second subscript is added to the above parameters to indicate the particular configuration. For example, for CE connection, the four parameters are written as  $h_{ie}$ ,  $h_{fe}$ ,  $h_{re}$ ,  $h_{oe}$ . Similarly, for CB connection, these are written as  $h_{ib}$ ,  $h_{fb}$ ,  $h_{rb}$  and for CC connection as  $h_{ic}$ ,  $h_{fc}$ ,  $h_{rc}$  and  $h_{oc}$ 

### The h-parameters of an Ideal CB Transistor

A CB-connected transistor has been shown in Fig.4 ( a ), connected in a black box. Fig.4 (b) gives its equivalent circuit. It should be noted that no external biasing resistors or any signal source has been shown connected to the transistor.



#### (i) Forward Parameters

The two forward h-parameters can be found from the circuit of Fig.4 ( a) where a short has been put across the output. The input impedance is simply  $r_e$ .

 $h_{ib} = r_e$ 

The output current equals the input current i.e. Since it flows out of the box, it is taken as negative. The forward current gain is

$$h_{fb} = \frac{-i_e}{i_e} = 1$$

(It also called the ac  $\alpha$  of the CB circuit.)

#### (ii) Reverse Parameters

The two reverse parameters can be found from the circuit diagram of Fig. ( b). When input terminals are open, there can be no ac emitter current. It means that ac current source (inside the box) has a value of zero and so appears as an 'open'. Because of this open, no voltage can appear across input terminals, however, large  $V_2$  may be. Hence,  $V_1$ =0.



 $\therefore \qquad h_{rb} \quad \frac{v_1}{v_2} \quad \frac{0}{v_2} \quad 0$ 

Similarly, the impedance, looking into the output terminals is infinite. Consequently, its admittance  $(= 1/\infty)$  is zero.

$$h_{ab} = 0$$

The four h-parameters of an ideal transistor connected in CB configuration are;

$$h_{ib} = r_e$$
;  $h_{fb} = -1$ ,  $h_{rb} = 0$ ;  $h_{ob} = 0$ 

The equivalent hybrid circuit is shown in Fig. 5.



In reality, output impedance is not infinity but very high so that  $h_{ob}$  is extremely small. Similarly, there is some amount of feedback between the output and the input

circuits (even when open) though it is very small. Hence, h is very small.

## The h--parameters of an ideal CE Transistor

Fig 6 (a) shows a CE-connected ideal transistor contained in a black box where shows its ac equivalent circuit in terms of its  $\beta$  and resistance values.



#### (a) Forward Parameters

The two forward h-parameters can be found from the circuit of Fig.7 (a) Where output has been shorted. Obviously, the input impedance is simply  $\beta r_e$ 

$$h_{ie} = \beta r_e$$

The forward current gain is given by

$$h_{fe} = \frac{i_2}{i_1} = \frac{i_b}{i_b}$$

(It is also called the ac beta of the CE circuit)

#### (b) Reverse Parameters

These can be found by reference to the circuit of Fig.7 (b), where input terminals are open but output terminals are driven by an are voltage source  $v_2$  With input terminals open, there can be no base current so that  $i_b = 0$ . If  $i_b = 0$ , then collector current source has zero value  $i_b$  and looks like an open. Hence, there can be no v due to this open.

1

$$\therefore \qquad h_{re} \quad \frac{v_1}{v_2} \quad \frac{0}{v_2} \quad 0$$

Again, the impedance looking into the output terminals is infinite so that conductance is zero  $\therefore$   $h_{oe} = 0$ .



Fig. 7.

Hence, the four h-parameters of an ideal transistor connected in CE transistor are

 $h_{ie} = \beta r_e; \quad h_{fe} = \beta, \quad hr_e = 0; \quad h_{oe} = 0.$ 

The hybrid equivalent circuit of such transistor is shown in fig.8.



# **Approximate Hybrid Equivalent Circuits**

(a) Hybrid CB Circuit

In Fig. 9. (a) is shown an NPN transistor connected in CB configuration. Its ac equivalent circuit employing h-parameters is shown in Fig. 9 (b).

The V/I relationships are given by the following two equations

$$v_{eb} = h_{ib} i_e + h_{rb} v_{cb}$$
$$i_e = h_{fb} i_e + h_{ob} v_{eb}$$

These equations are self-evident because applied voltage across input terminals must equal the drop over  $h_{ib}$  and the generator voltage. Similarly, current  $i_c$  the output terminals must equal the sum of two branch currents.



#### (b) Hybrid CE Circuit

The hybrid equivalent of the transistor alone when connected in CE configuration is shown in Fig.10 (b). Its V/I characteristics are described by the following two equations.



#### (c) Hybrid CC Circuit

The hybrid equivalent of a transistor alone when connected in CC Configuration is shown in Fig.11( b). Its V/I characteristics are defined by the following two equations :



We may connect signal input source across output terminals BC and load resistance across output terminals EC to get a CC amplifier.

# **Typical Values of Transistor h-parameters**

In the table below are given typical values for each parameter for the broad range of transistors available today in each of the three configurations.

Parameter	CB	CE	CC
h <sub>i</sub>	25 Ω	1 K	1 K
h <sub>r</sub>	$3 \times 10^{-4}$	$2.5  imes 10^{-4}$	≅ 1
$h_f$	-0.98	50	-50
$h_o$	$0.5  imes 10^{-6} \mathrm{S}$	$25 \times 10^{-6} \mathrm{S}$	$25  imes 10^{-6} \mathrm{S}$

# Approximate Hybrid Formulas

The approximate hybrid formulas for the three connections are listed below. These are applicable when  $h_o$  and  $h_r$  is very small and R <sub>s</sub> is very large. The given values refer to transistor terminals. The values of  $r_{in(stage)}$  or  $r_{in}$  and  $r_{o(stage)}$  will depend on biasing resistors and load resistance respectively.

Item	CE	СВ	CC
r <sub>in</sub>	h <sub>ie</sub>	h <sub>ib</sub>	$h_{ic} + h_{fe}R_L$
ю	$\frac{1}{h_{oc}}$	$\frac{1}{h_{oB}}$	$rac{h_{ie}}{h_{fc}}$
$A_i$	$h_{fe} = \beta$	$-h_{fb} \cong 1$	$-h_{fe} \cong \beta$
$A_{v}$	$\frac{h_{ie}R_C}{h_{is}}$	$\frac{f_{fb}}{h_{ib}}R_C$	1

# **Common Emitter h-parameter Analysis**

The h-parameter equivalent of the CE circuit of Fig.12, no emitter resistor has been connected.



Fig. 13

We will now derive expressions for voltage and current gains for both these circuits.

#### 1. Input Impedance

When looking into the base-emitter terminals of the transistor,  $h_{ie}$  in series with  $h_{re}$  no. For a CE circuit,  $h_{re}$  is very small so that  $h_{re} V_o$  is negligible as compared to the drop over  $h_{ie}$ . Hence,  $r_{in}=h_{ie}$ .

Now, consider the circuit of Fig.13. Again ignoring  $h_{re} V_o$  we have

$$v_{I} = h_{ie}i_{b} + i_{e}R_{E} = h_{ie}i_{b} + (i_{b} + i)R_{E}$$
  
=  $h_{ie}i_{b} + i_{b}R_{E} + h_{fe}i_{b}R_{E}$  ((  $i_{c} + h_{fe}i_{b}$ )  
=  $i_{b}[h_{ie} + R_{E}(1 + h_{fe})]$   
∴  $r_{in} = r_{in(base)} = \frac{v_{1}}{i_{1}} \frac{v_{1}}{i_{b}} h_{ie}$  (1  $h_{fe})R_{E} * $r_{in} \text{ or } r_{in(base)} = R_{1} ||R_{2}||r_{in(base)}$$ 

#### 2. Output Impedance

Looking back into the collector and emitter terminals of the transistor in Fig. (12 b),  $r_0 = l/h_{oe}$ .

As seen,  $r_o'$  or  $r_{o(stage)} = r_o || R_L = (1/h_o) || r_L$  ( $r_L R_L$ ) Since  $1/h_{oe}$  is typically 1 M or so and  $R_L$  is usually much smaller,  $r_o' \cong R_L = r_L$ 

#### 3. Voltage Gain

 $A_{v} \quad \frac{v_{2}}{v_{1}} \quad \frac{v_{o}}{v_{in}}$ 

Now,  $v_o = -i_c R_L$  and  $v_{in} \cong i_b h_{ie}$ 

$$\therefore \quad A_{v} \quad \frac{i_{s}R_{L}}{i_{b}h_{ie}} \quad \frac{i_{c}}{i_{b}} \cdot \frac{R_{L}}{h_{ie}} \quad \frac{h_{f}R_{L}}{h_{ie}}$$

Now, consider Fig.13( b). Ignoring  $h_{re}v_o$ , we have from the input loop of the circuit  $v_{in} = i_b [h_{ie} + R_E (1 + h_{fe})]$  -proved above

$$\therefore \quad A_{v} \quad \frac{v_{o}}{v_{in}} \quad \frac{i_{c}R_{L}}{i_{b}[h_{ie} \quad R_{E}(1 \quad h_{fe})]} \quad \frac{h_{fe}R_{L}}{h_{fe} \quad (1 \quad h_{fe})R_{E}}$$

$$\frac{R_{L}}{R_{E}} \qquad \qquad - \operatorname{if}(1+h_{fe})R_{E} >> h_{ie}$$

# 4. Current Gain

$$\begin{array}{ll} A_{i} & \frac{i_{2}}{i_{1}} & \frac{h_{fe}}{1 & h_{oe}r_{L}} & h_{fe} & & \\ A_{is} & \frac{h_{fe} \cdot R_{1} \|R_{2}}{r_{in} & R_{1} \|R_{2}} \end{array} & & \\ \end{array}$$

5. Power Gain

$$A_{\rm p} = A_{\rm v} \times A_i$$

# **Common Collector h-parameter Analysis**

The CC transistor circuit and its h-parameter equivalent are shown in Fig.14





# 1. Input Impedance

$$\begin{aligned} v_{in} &= i_b h_{ic} + h_{rc} v_o = i_b h_{ic} + v_o = i_b h_{ic} + i_e R_L \\ &= i_b h_{ic} + h_{fe} i_b R_L = i_b (h_{ic} + h_{fe} R_L) \\ \therefore & r_{in} \quad \frac{v_{in}}{i_b} \quad h_{ic} \quad h_{fe} R_L \end{aligned}$$

$$As seen, \quad r_{in(stage)} = r_{in(base)} || R_1 || R_2 = r_{in(base)} || R_B \text{ where } R_B = R_1 || R_2 \end{aligned}$$

# 2. Output Impedance

$$r_o \quad \frac{v_2}{i_2} \mid_{v_s = 0} \qquad \qquad \frac{v_o}{i_c} \mid_{v_s = 0}$$

Now,  $i_e \cong i_c = h_{fe} i_b = h_{fc} i_l$ Since  $v_s = 0$ ,  $i_b$  is produced by  $h_{rc} v_o = v_o$ 

Hence, considering the input circuit loop, we get

$$i_{b} \quad \frac{v_{0}}{h_{ic}} \quad \frac{v_{0}}{(R_{S} \parallel R_{1} \parallel R_{2})} \quad \frac{v_{0}}{h_{ic}}$$

$$i_{c} \quad h_{fc} \quad i_{b} \quad \frac{h_{fc} \quad v_{o}}{h_{ic}} \quad (R_{S} \parallel R_{B})$$
where  $R_{B} = R_{1} \parallel R_{2}$ 

$$\therefore \qquad r_o \quad \frac{V_o}{i_e} \quad \frac{h_{ic} \quad (R_S \parallel R_1 \parallel R_2)}{h_{fe}}$$

Also,  $r_o'$  or  $r_{o(stage)} = r_o || R_L$ 3. Voltage Gain

$$A_{v} \quad \frac{v_{2}}{v_{1}} \quad \frac{v_{o}}{v_{in}}$$
Now,  $v_{o} = i_{e} R_{L} = h_{fe} i_{b} R_{L}$  and  $i_{b} = (v_{in} - v_{o}) / h_{ic}$ 

$$v_{o} \quad \frac{h_{fe} R_{L}}{h_{ie}} (v_{in} \quad v_{o}) \quad \text{or} \quad v_{o} \quad 1 \quad \frac{h_{fe} R_{L}}{h_{ic}} \quad \frac{h_{fe} R_{L} v_{in}}{h_{ic}}$$

$$\therefore \qquad A_{v} \quad \frac{v_{o}}{h_{v}} \quad \frac{h_{fe} R_{L} / h_{ic}}{h_{ic}} \quad 1$$

$$\therefore \qquad A_{v} \quad \frac{V_{o}}{v_{in}} \quad \frac{h_{fe}R_{L}/h_{ic}}{1 \quad h_{fe}R_{L}/h_{ic}}$$

4. Current Gain

$$A_i \quad \frac{i_2}{i_1} \quad \frac{i_e}{i_b} \quad h_{fe}; A_{is} \quad \frac{h_{fe}R_B}{r_{in} \quad R_B} \qquad \text{where } R_B = R_1 || R_2$$